

# Proiect Cia

Componenta: Suciu Vlad


Tasca Andrei-Antonio

Cerinte de proiectare:


Amplificator diferential	Topologie	Amplificator diferential de tip N cu sarcina oglinda
	Produs amplificare-banda [MHz]	30
	Capacitate de sarcina [pF]	6
Sursa de curent	Topologie	Sursa de curent cu tranzistor PMOS cu degenerare rezistiva
	Curent de iesire [uA]	15
	Tensiune de iesire minima [mV]	400
Oglinda de curent	Topologie	Oglinda/oglinzi de curent cascode

Circuite:



- Sursa de curent

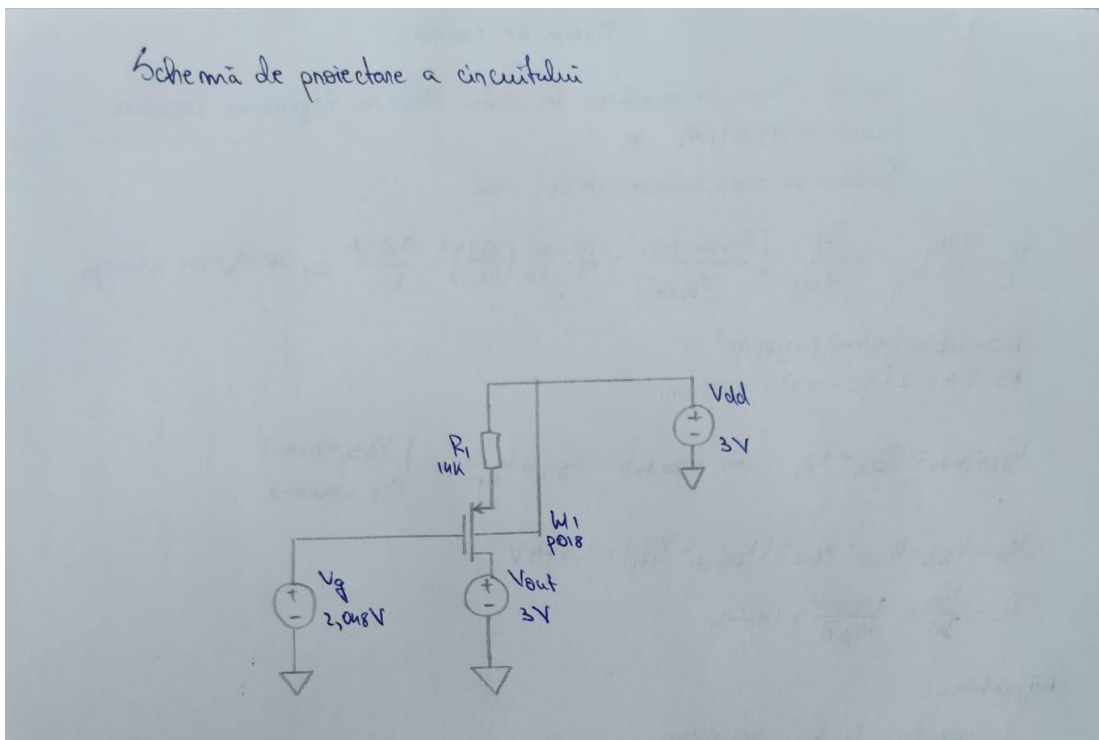

- Amplificator diferential

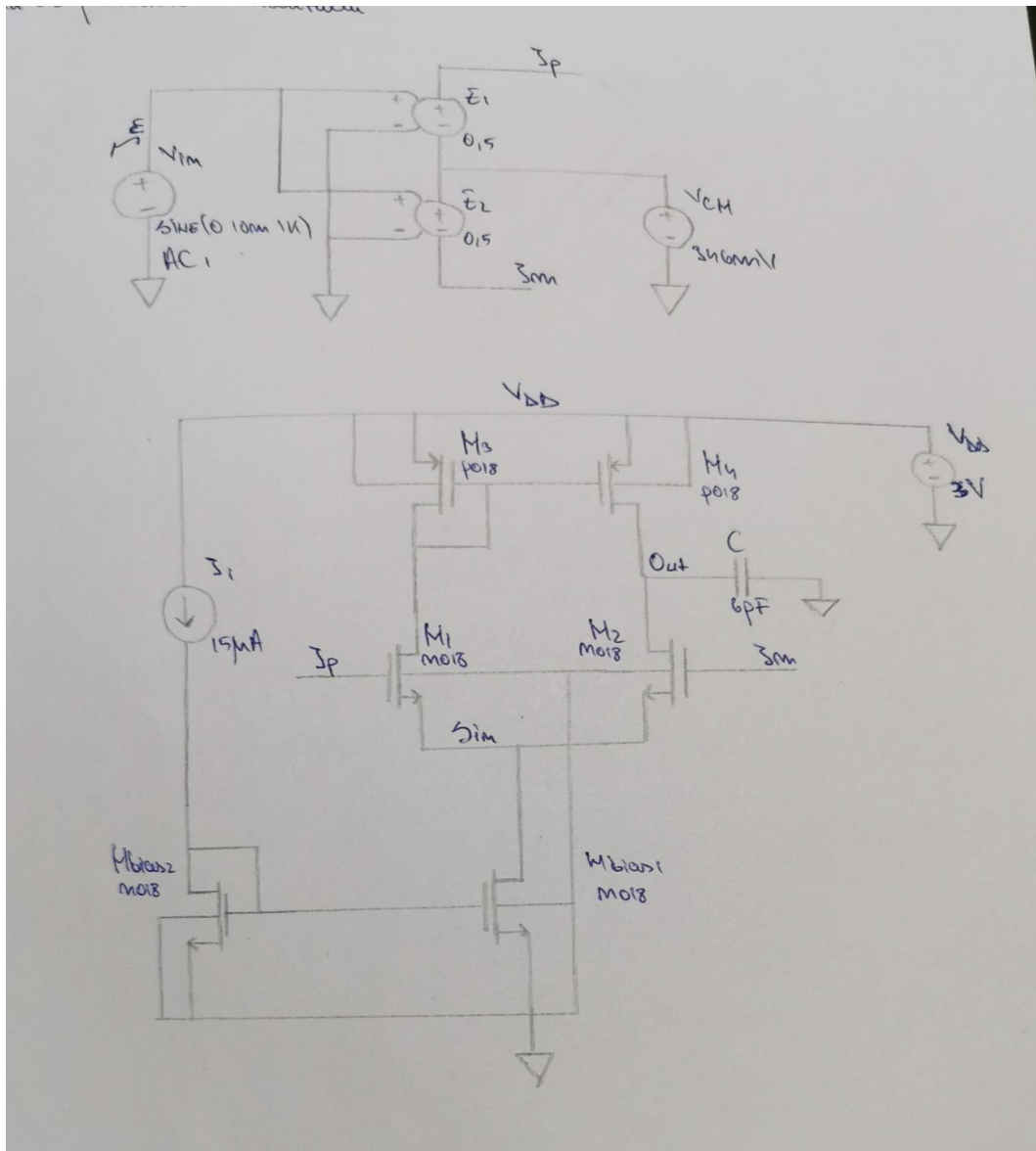


- Oglinzi cascode

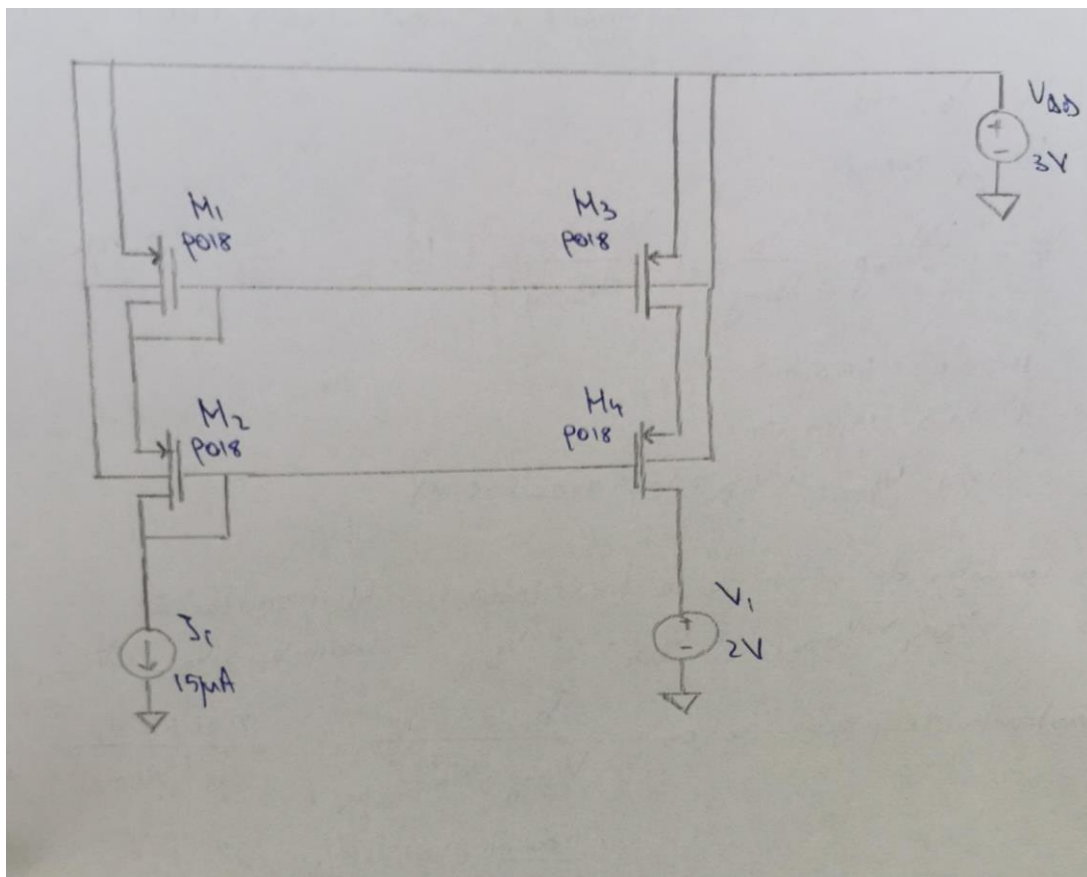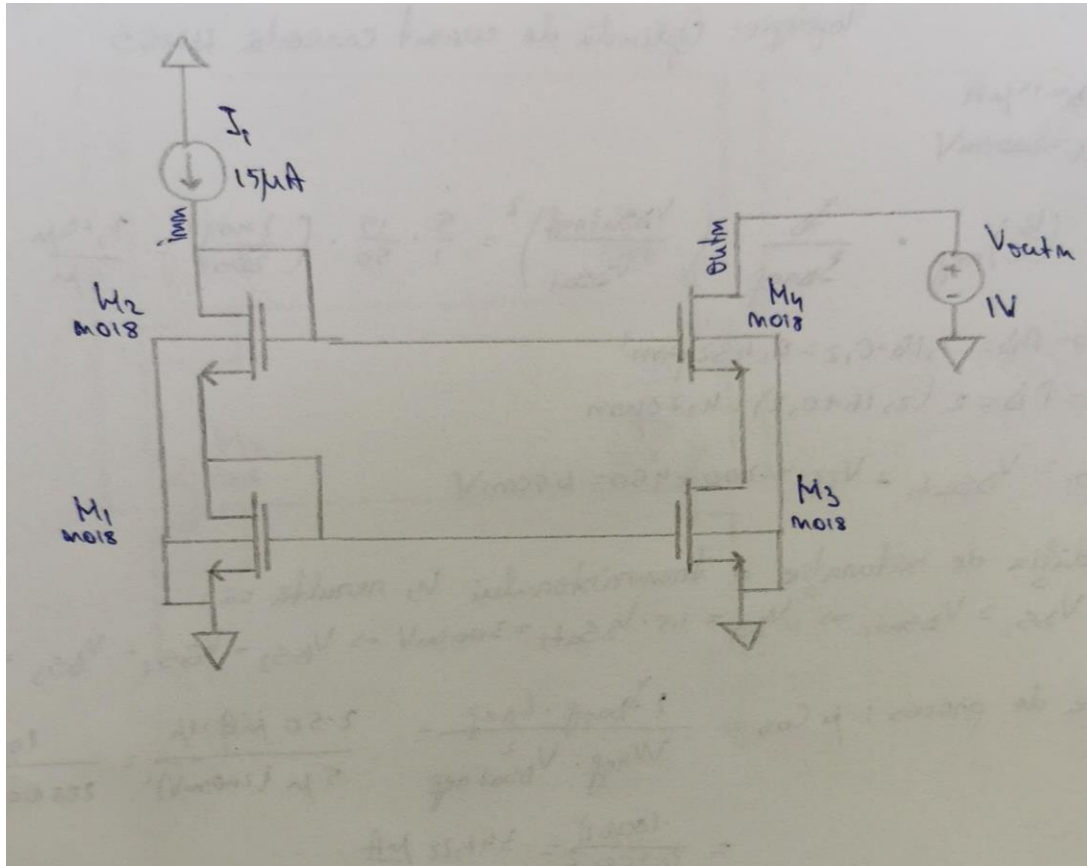

# Raport sursa de curent

- Schema electrica la nivel de transistor a sursei de curent

.lib 180nmL7.lib

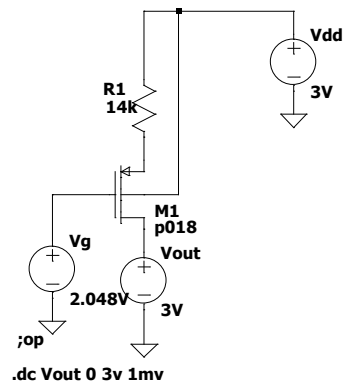

- Proiectarea circuitului după specificații (Iout și Vout)

Sursa de curent

Topologie: Sursa de curent cu tranzistor PMOS cu degenerare rezistivă  
 Curent de ieșire [μA]: 15  
 Tensiune de ieșire minimă [mV]: 400

$$\frac{W}{L} = \left(\frac{W}{L}\right)_{\text{ref}} \cdot \frac{I_D}{I_{D,\text{ref}}} \cdot \left(\frac{V_{DS,\text{sat}} + V_{DS,\text{ref}}}{V_{DS,\text{sat}}}\right)^2 = \frac{15}{1} \cdot \frac{15}{50} \cdot \left(\frac{257}{180}\right)^2 = \frac{9,04 \mu\text{m}}{1 \mu\text{m}} \Rightarrow W = 9,04 \mu\text{m}, L = 1 \mu\text{m}$$

$$A_S = A_D = 9,04 \cdot 0,2 = 1,8 \mu\text{m}^2$$

$$P_S = P_D = 2(9,04 + 0,2) = 18,48 \mu\text{m}$$

$$V_{G_S} = V_{DS_1} + V_{R_1} \quad (\Rightarrow) \quad 400 \text{ mV} = V_{DS_1} + V_{R_1} \Rightarrow \begin{cases} V_{DS_1} = 210 \text{ mV} \\ V_{R_1} = 190 \text{ mV} \end{cases}$$

$$V_G = V_{DD} - V_{GS} = V_{DD} - (V_{DS,\text{sat}} + V_{Th}) = 2,374 \text{ V}$$

$$R_1 = \frac{V_{R_1}}{I_D} = \frac{210 \text{ mV}}{15 \mu\text{A}} = 14 \text{ k}\Omega$$

Adjustări:

- pentru  $M_1 \rightarrow$

$$W = 8,23 \mu\text{m}$$

$$A_S = A_D = 1,64 \mu\text{m}^2$$

$$P_S = P_D = 16,86 \mu\text{m}$$

-  $V_G = 2,5048 \text{ V}$

Tranzistor	W/L	$I_D$	$V_{DS,\text{sat}}$	$V_{DS}$	$V_{Th}$	$V_{GS}$	$g_m$	$g_{DS}$
$M_1$	$8,23 \mu\text{m} / 1 \mu\text{m}$	$15 \mu\text{A}$	$180 \text{ mV}$	$2,79 \text{ V}$	$504 \text{ mV}$	$742 \text{ mV}$	$122 \mu\text{S}$	$1,47 \mu\text{S}$


Calculat:  $R_{out} = r_{DS} + R + (g_m + g_{mb}) r_{DS} R = 680 \text{ k}\Omega + 14 \text{ k}\Omega + (122 \mu\text{S} + 31 \mu\text{S}) 680 \text{ k}\Omega \cdot 14 \text{ k}\Omega = 2,034 \text{ M}\Omega$

$$r_{DS} = \frac{1}{g_{DS}} = 0,680 \cdot 10^6 = 680 \text{ k}\Omega$$

Măsurat:  $R_{out} = \frac{1}{5,8} \cdot 10^7 = 0,172 \cdot 10^7 = 1,72 \text{ M}\Omega$

Parametru	Calculat	Măsurat
$R_{out}$	$2,034 \text{ M}\Omega$	$1,72 \text{ M}\Omega$

Schema de proiectare a circuitului

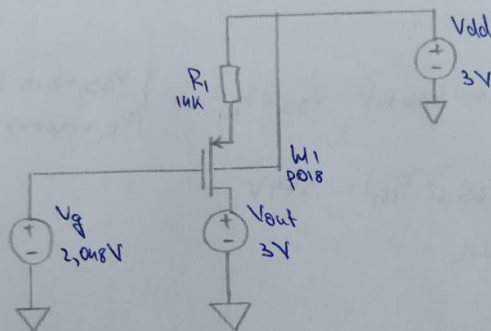


- Error log inainte de ajustare

```
SPICE Error Log: C:\Users\ASUS\OneDrive\Desktop\cia\Proiect_noi\sursa de curent\srs-cascoda-MOS.log
Circuit: * C:\Users\ASUS\OneDrive\Desktop\cia\Proiect_noi\sursa de curent\srs-cascoda-MOS.asc
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
    --- BSIM3 MOSFETS ---
Name:      n1
Model:     p018
Id:        -1.78e-05
Vgs:       -7.61e-01
Vds:       -2.75e+00
Vbs:       2.49e-01
Vth:       -5.14e-01
Vdsat:     -1.87e-01
Gm:        1.38e-04
Gds:       1.73e-06
Gmb:       3.45e-05
Cbd:       1.45e-14
Cbs:       2.59e-14
Cgssov:    4.92e-15
Cgsdov:    4.23e-15
Cgbsov:    0.00e+00
dQgdVgb:   6.65e-14
dQgdVdb:   -4.23e-15
dQgdVsb:   -5.92e-14
dQddVgb:   -4.23e-15
dQddVdb:   1.88e-14
dQddVsb:   4.70e-18
dQbdVgb:   -1.12e-14
dQbdVdb:   -1.45e-14
dQbdVsb:   -2.98e-14

Date: Tue May 10 12:43:15 2022
Total elapsed time: 0.075 seconds.


tnom = 27
temp = 27
method = trap
totiter = 5
traniter = 0
tranpoints = 0
accept = 0
rejected = 0
matrix size = 5
fillins = 0
solver = Normal
Matrix Compiler1: 150 bytes object code size
Matrix Compiler2: 329 bytes object code size
```

- Caracteristica de iesire

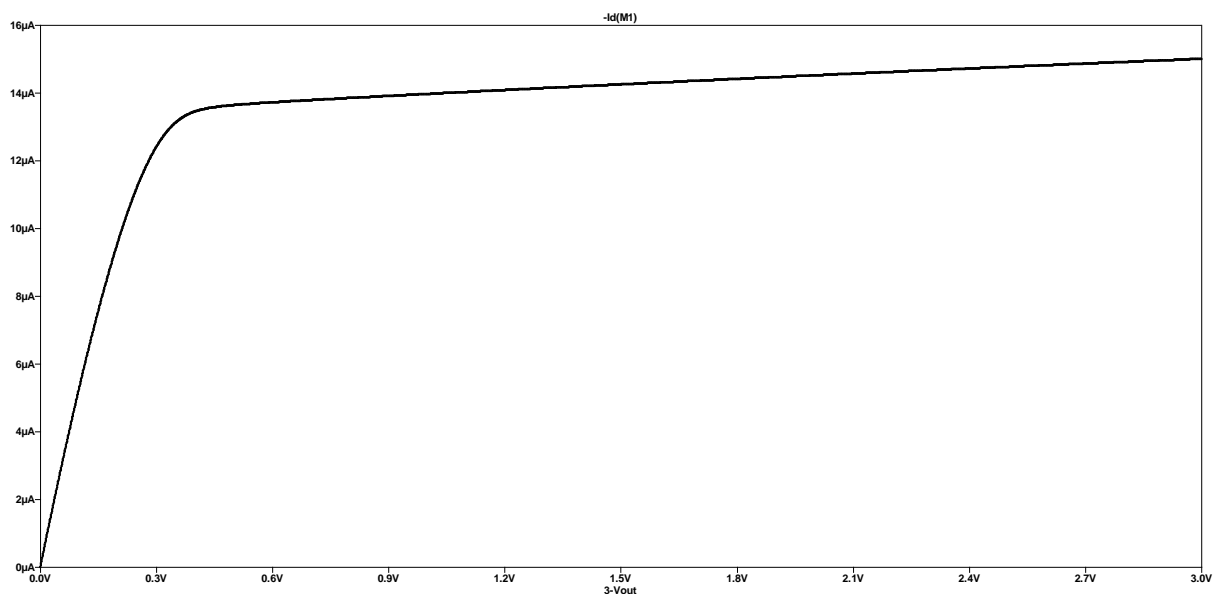
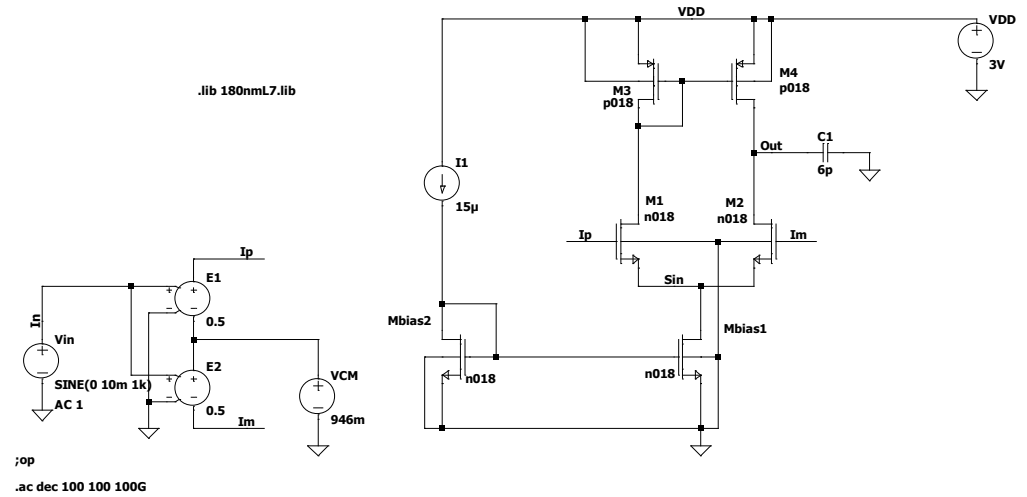
# Raport amplificator differential

- Schema electrica la nivel de transistor al amp. differential





- Proiectarea circuitului după specificații (GBW și CL)

### Amplificator diferențial

Topologie: Amplificator diferențial de tip H cu sarcină oglindă

Produs amplificare-banda [MHz]: 30

Capacitate de sarcină [pF]: 6

$$GBW > 30 \Rightarrow GBW = 50 \text{ MHz}, C_L = 6 \text{ pF}, I_{out} = 15 \mu A$$

$$G_m = 2 \pi GBW C_L = 2 \pi \cdot 50 \cdot 10^6 \cdot 6 \cdot 10^{-12} = 1884 \mu S = 1,88 \text{ mS}$$

$$V_{DSat} = 200 \text{ mV}$$

$$g_{m1} = \frac{2I_D}{V_{DSat}}, g_m = 2GBW = 2 \cdot 1,88 \text{ mS} = 3,76 \text{ mS}$$

$$I_{D1,2} = \frac{g_{m1} V_{DSat}}{2} = \frac{3,76 \text{ mS} \cdot 200 \text{ mV}}{2} = 376 \mu A$$

$$\left(\frac{W}{L}\right)_{1,2} = \left(\frac{W}{L}\right)_{ref} \cdot \frac{I_D}{I_{Dref}} \left(\frac{V_{DSatref}}{V_{DSat}}\right)^2 = \frac{5}{1} \cdot \frac{376}{50} \cdot \left(\frac{240}{200}\right)^2 = \frac{54,14 \mu}{1 \mu} \Rightarrow \begin{cases} W = 54,14 \mu \\ L = 1 \mu \end{cases}$$

$$A_S = A_D = 10,82 \text{ pm}^2$$

$$P_S = P_D = 108,68 \mu m$$

$$\left(\frac{W}{L}\right)_{3,4} = \left(\frac{W}{L}\right)_{ref} \cdot \frac{I_D}{I_{Dref}} \left(\frac{V_{DSatref}}{V_{DSat}}\right)^2 = \frac{5}{1} \cdot \frac{376}{50} \cdot \left(\frac{257}{200}\right)^2 = \frac{183,86 \mu}{1 \mu} \Rightarrow \begin{cases} W = 183,86 \mu \\ L = 1 \mu \end{cases}$$

$$A_S = A_D = 36,77 \text{ pm}^2$$

$$P_S = P_D = 368,12 \mu m$$

$$\left(\frac{W}{L}\right)_{Bias1} = \left(\frac{W}{L}\right)_{ref} \cdot \frac{I_D}{I_{Dref}} \left(\frac{V_{DSatref}}{V_{DSat}}\right)^2 = \frac{5}{1} \cdot \frac{15}{50} \cdot \left(\frac{240}{200}\right)^2 = \frac{2,16 \mu}{1 \mu} \Rightarrow \begin{cases} W = 2,16 \mu \\ L = 1 \mu \end{cases}$$

$$A_S = A_D = 9,43 \text{ pm}^2$$

$$P_S = P_D = 4,72 \mu m$$

$$I_{DBias1} = I_{D1,2} + I_{D3,4} = 752 \mu A$$

$$\left(\frac{W}{L}\right)_{Bias1} = \left(\frac{W}{L}\right)_{ref} \cdot \frac{I_D}{I_{Dref}} \left(\frac{V_{DSatref}}{V_{DSat}}\right)^2 = \frac{5}{1} \cdot \frac{752}{50} \cdot \left(\frac{240}{200}\right)^2 = \frac{108,28 \mu}{1 \mu} \Rightarrow \begin{cases} W = 108,28 \mu \\ L = 1 \mu \end{cases}$$

$$A_S = A_D = 21,65 \text{ pm}^2$$

$$P_S = P_D = 216,96 \mu m$$

$$V_{CH} = V_{GS1,2} + V_{DSBias1} = V_{DSat1,2} + V_{TH} + V_{DSBias1} = 200 + 446 + 300 = 946 \text{ mV}$$

$$V_{DSBias1} = V_{DSat} + \Delta V = 200 + 100 = 300 \text{ mV}$$

Modifikasi

Ajustasi:

- pentan Mbiass  $\rightarrow W/L = 115,5 \mu$

$A_S = A_D = 23,1 \mu m^2$

$P_S = P_D = 231,4 \mu m$

Transistor	$W/L$	$I_D$	$V_{DSat}$	$V_{GS}$	$V_{th}$	$V_{GS}$	$g_m$	$g_{DS}$
$M_1$	$54,14 \mu / 1 \mu$	$376 \mu A$	$138 mV$	$2,04 V$	$511 mV$	$719 mV$	$2,90 mS$	$29,9 \mu S$
$M_2$	$54,14 \mu / 1 \mu$	$376 \mu A$	$138 mV$	$2,04 V$	$511 mV$	$719 mV$	$2,90 mS$	$29,9 \mu S$
$M_3$	$183,86 \mu / 1 \mu$	$376 \mu A$	$205 mV$	$732 mV$	$446 mV$	$732 mV$	$2,56 mS$	$46 \mu S$
$M_4$	$183,86 \mu / 1 \mu$	$376 \mu A$	$205 mV$	$732 mV$	$446 mV$	$732 mV$	$2,56 mS$	$46 \mu S$
Mbiass1	$115,5 \mu / 1 \mu$	$752 \mu A$	$203 mV$	$227 mV$	$446 mV$	$665 mV$	$5,52 mS$	$448 \mu S$
Mbiass2	$2,16 \mu / 1 \mu$	$15 \mu A$	$203 mV$	$665 mV$	$446 mV$	$665 mV$	$114 \mu S$	$1,38 \mu S$

$$A_0 = g_{m1} (\frac{1}{g_{DS2}} \parallel \frac{1}{g_{DS4}}) = g_{m1} \cdot \frac{g_{DS2} \cdot g_{DS4}}{g_{DS2} + g_{DS4}} = 2,90 \cdot 10^{-3} \cdot \frac{13,15 \cdot 10^{-3}}{13,15 \cdot 10^{-3} + 21,7 \cdot 10^{-3}} = 38,13$$

$$g_{DS2} = \frac{1}{r_{DS2}} = \frac{1}{29,9} \cdot 10^6 = 0,0334 \cdot 10^6 = 33,4 K\Omega$$

$$g_{DS4} = \frac{1}{r_{DS4}} = \frac{1}{46} \cdot 10^6 = 0,0217 \cdot 10^6 = 21,7 K\Omega$$

Sn deribeti:  $20 \log A_0 = 20 \log 38,13 = 20 \cdot 1,58 = 31,6 dB$

$$R_{out} = r_{DS2} \parallel r_{DS4} = 13,15 K\Omega$$

$$GBW = \frac{g_{m1}}{2\pi C_L} = \frac{2,90 \cdot 10^{-3}}{2\pi \cdot 23,14 \cdot 10^{-12}} = 0,0769 \cdot 10^9 = 76,9 MHz$$

$$BW = \frac{1}{2\pi R_{out} C_L} = \frac{1}{2\pi \cdot 13,15 \cdot 10^3 \cdot 6 \cdot 10^{-12}} = \frac{1}{495,5 \cdot 10^{-9}} = 0,00201 \cdot 10^9 = 2,01 MHz$$



$$f_{p1} = BW = 2,01 MHz$$

$$f_{p2} = \frac{g_{m3}}{2\pi C_L} = \frac{2,56 \cdot 10^{-3}}{2\pi \cdot 23,14 \cdot 10^{-12}} = 0,0679 \cdot 10^9 = 67,9 MHz$$

Parameter	Calculated	Measured
$A_0$	31,6 dB	31,57 dB
$f_{pol}$	2,01 MHz	1,76 MHz
$GBW$	76,9 MHz	62,65 MHz

## Amplificator diferential

Schema de proiectare a circuitului

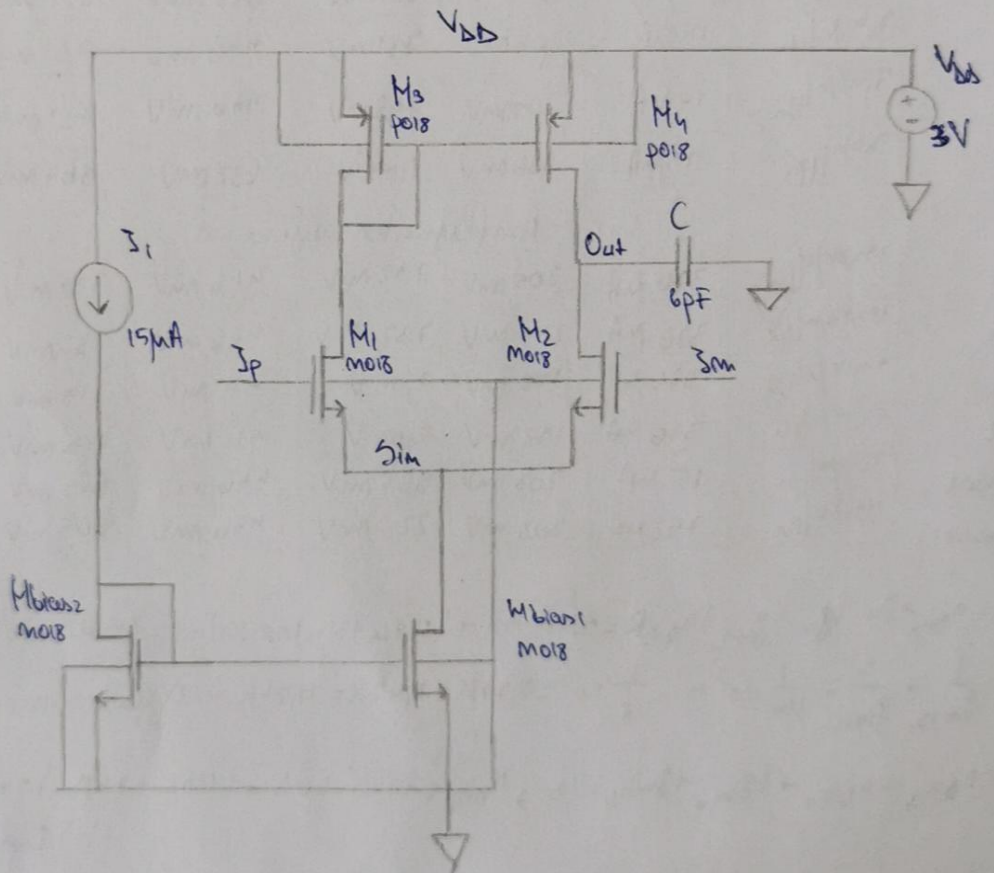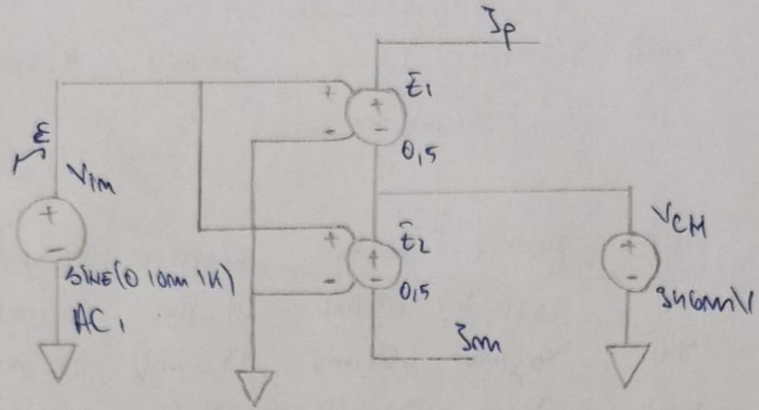



## • Error log inainte de ajustare

SPICE Error Log: C:\Users\ASUS\OneDrive\Desktop\cia\Proiect\_noi\amplificator\ampdif-sarcsrs.log

Circuit: \* C:\Users\ASUS\OneDrive\Desktop\cia\Proiect\_noi\amplificator\ampdif-sarcsrs.asc

Direct Newton iteration for .op point succeeded.

Semiconductor Device Operating Points:

```
--- BSIM3 MOSFETS ---
Name:      m3      m4      mbias2      m2      mbias1
Model:     p018    p018    n018      n018    n018
Id:        -3.54e-04 -3.54e-04  1.50e-05  3.54e-04  7.08e-04
Vgs:       -7.24e-01 -7.24e-01  6.65e-01  7.13e-01  6.65e-01
Vds:       -7.24e-01 -7.24e-01  6.65e-01  2.04e+00  2.33e-01
Vbs:       0.00e+00  0.00e+00  0.00e+00 -2.33e-01  0.00e+00
Vth:       -4.46e-01 -4.46e-01  4.46e-01  5.13e-01  4.46e-01
Vdsat:     -1.99e-01 -1.99e-01  2.03e-01  1.92e-01  2.03e-01
Gm:        2.50e-03  2.50e-03  1.14e-04  2.82e-03  5.22e-03
Gds:       4.37e-05  4.37e-05  1.38e-06  2.84e-05  3.73e-04
Gmb:       6.77e-04  6.77e-04  3.64e-05  8.28e-04  1.67e-03
Cbd:       4.37e-13  4.37e-13  4.30e-15  7.79e-14  2.29e-13
Cbs:       5.81e-13  5.81e-13  5.30e-15  1.15e-13  2.50e-13
Cgssov:    1.00e-13  1.00e-13  1.18e-15  2.95e-14  5.91e-14
Cgdov:     9.90e-14  9.90e-14  1.17e-15  2.61e-14  5.90e-14
Cgbvov:    0.00e+00  0.00e+00  0.00e+00  0.00e+00  0.00e+00
dqgdVgb:   1.38e-12  1.38e-12  1.60e-14  3.95e-13  8.17e-13
dqgdVdb:   -9.94e-14 -9.94e-14 -1.17e-15 -2.61e-14 -7.52e-14
dqgdVab:   -1.21e-12 -1.21e-12 -1.39e-14 -3.48e-13 -6.98e-13
dqddVgb:   -1.01e-13 -1.01e-13 -1.20e-15 -2.61e-14 -9.51e-14
dqddVdb:   5.38e-13  5.38e-13  5.48e-15  1.04e-13  3.28e-13
dqddVab:   1.40e-15  1.40e-15  2.37e-17  5.50e-17  6.99e-15
dqbdVgb:   -2.37e-13 -2.37e-13 -2.29e-15 -5.55e-14 -1.06e-13
dqbdVdb:   -4.38e-13 -4.38e-13 -4.30e-15 -7.79e-14 -2.40e-13
dqbdVab:   -6.85e-13 -6.85e-13 -7.43e-15 -1.59e-13 -3.59e-13
```


```
Name:      m1
Model:     n018
Id:        3.54e-04
Vgs:       7.13e-01
Vds:       2.04e+00
Vbs:       -2.33e-01
Vth:       5.13e-01
Vdsat:     1.92e-01
Gm:        2.82e-03
Gds:       2.84e-05
Gmb:       8.28e-04
Cbd:       7.79e-14
Cbs:       1.15e-13
Cgssov:    2.95e-14
Cgdov:     2.61e-14
Cgbvov:    0.00e+00
dqgdVgb:   3.95e-13
dqgdVdb:   -2.61e-14
dqgdVab:   -3.48e-13
dqddVgb:   -2.61e-14
dqddVdb:   1.04e-13
dqddVab:   5.50e-17
dqbdVgb:   -5.55e-14
dqbdVdb:   -7.79e-14
dqbdVab:   -1.59e-13
```

```
Name:      n1
Model:     n018
Id:        3.54e-04
Vgs:       7.13e-01
Vds:       2.04e+00
Vbs:       -2.33e-01
Vth:       5.13e-01
Vdsat:     1.92e-01
Gm:        2.82e-03
Gds:       2.84e-05
Gmb:       8.28e-04
Cbd:       7.79e-14
Cbs:       1.15e-13
Cgssov:    2.95e-14
Cgdov:     2.61e-14
Cgbvov:    0.00e+00
dqgdVgb:   3.95e-13
dqgdVdb:   -2.61e-14
dqgdVab:   -3.48e-13
dqddVgb:   -2.61e-14
dqddVdb:   1.04e-13
dqddVab:   5.50e-17
dqbdVgb:   -5.55e-14
dqbdVdb:   -7.79e-14
dqbdVab:   -1.59e-13
```

Date: Tue May 10 13:41:43 2022  
Total elapsed time: 0.060 seconds.

```
tnom = 27
temp = 27
method = trap
totiter = 6
traniter = 0
tranpoints = 0
accept = 0
rejected = 0
matrix size = 14
fillins = 0
solver = Noxmal
Matrix Compiler1: 518 bytes object code size
Matrix Compiler2: 1.03 KB object code size
```



- Caracteristica de modul si faza

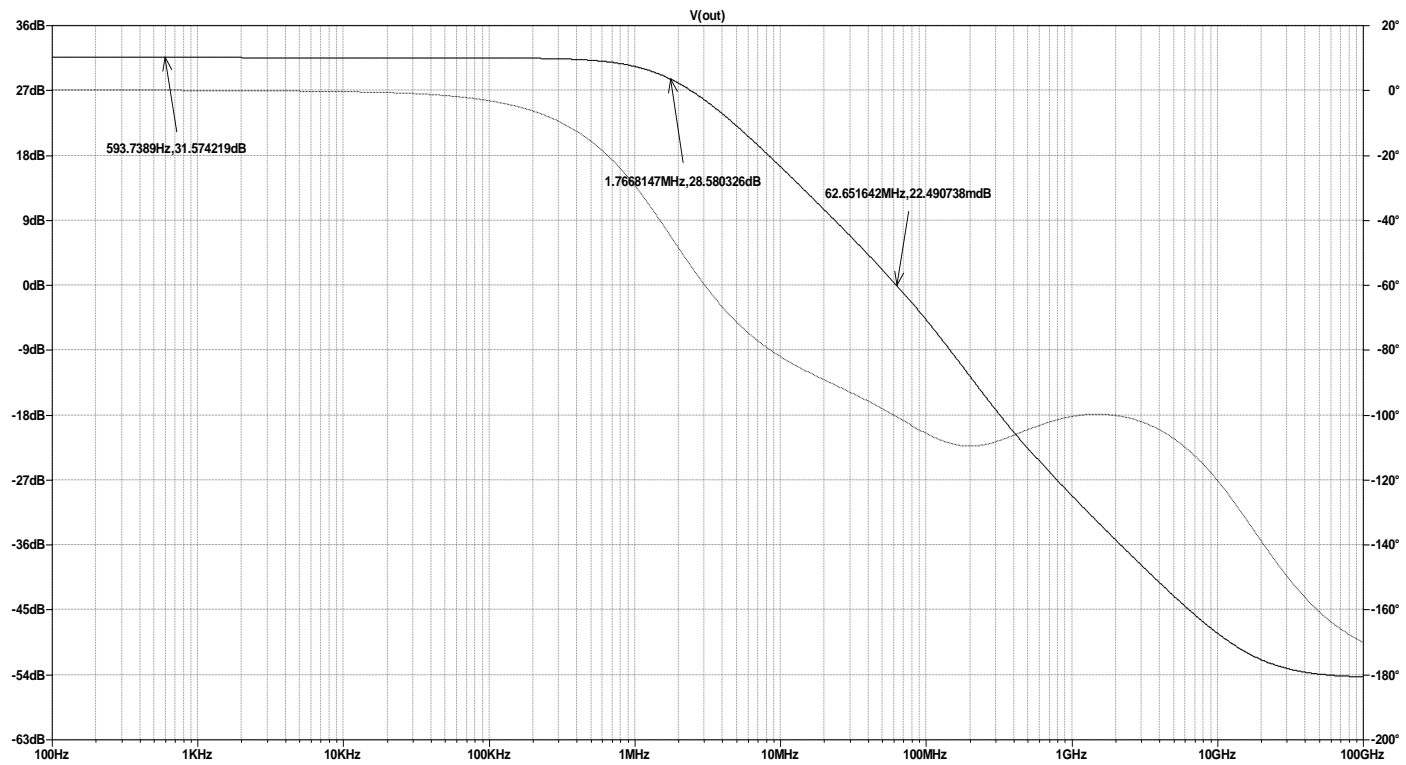


# Raport oglinzi de curent
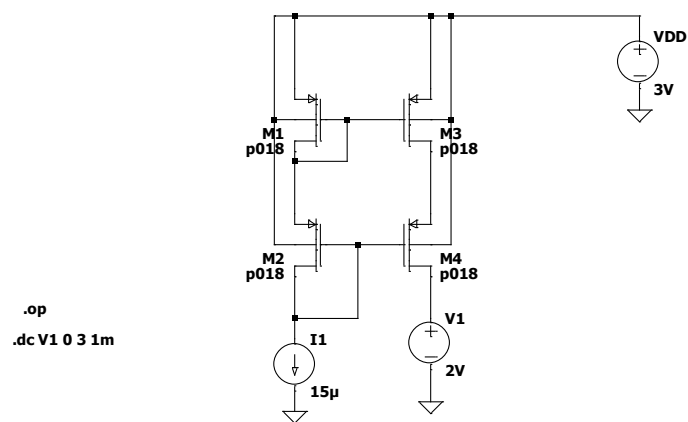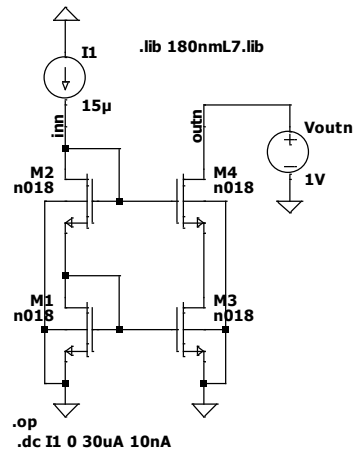
## NMOS

- Schema electrica la nivel de transistor a structurii de oglinzi



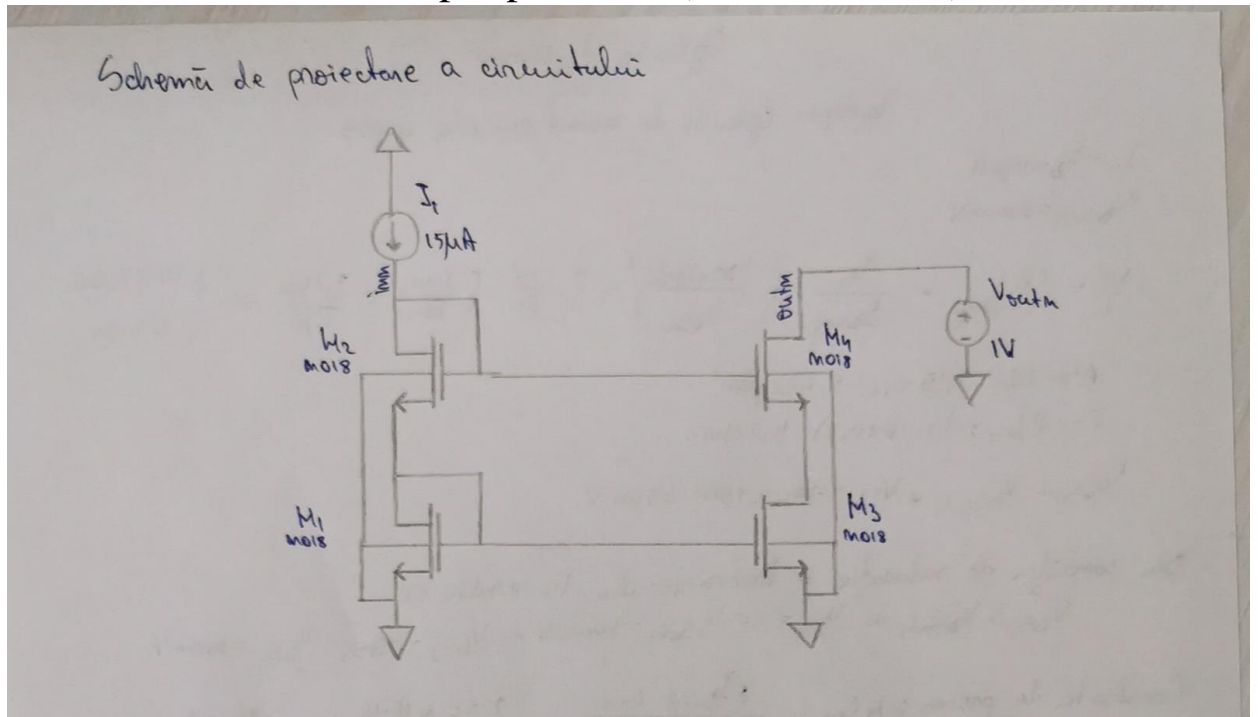- Proiectarea circuitului după specificații ( $I_{in}$ ,  $I_{out}$ ,  $V_{dsat}$ )



## Oglindă de curent

Topologie: Oglindă de curent cascadă NMOS

$$I_{in} = I_D = 15 \mu A$$

$$V_{DSat} = 200 mV$$

$$\frac{W}{L} = \left(\frac{W}{L}\right)_{ref} \cdot \frac{I_D}{I_{Dref}} \cdot \left(\frac{V_{DSatref}}{V_{DSat}}\right)^2 = \frac{5}{1} \cdot \frac{15}{50} \cdot \left(\frac{200}{200}\right)^2 = \frac{3,16 \mu}{1 \mu} \Rightarrow \begin{cases} W = 3,16 \mu \\ L = 1 \mu \end{cases}$$

$$AS = AD = 3,16 \cdot 0,2 = 0,432 \mu m^2$$

$$PS = PD = 2(3,16 + 0,2) = 4,72 \mu m$$

$$V_{GS1} = V_{DSat1} + V_{Th} = 200 + 450 = 650 mV$$

În condiția de naturatie a tranzistorului  $M_1$  rezultă că:

$$V_{DS1} > V_{DSat1} \Rightarrow V_{DS1} = 1,5 \cdot V_{DSat1} = 300 mV \Rightarrow V_{DS3} - V_{GS1} - V_{DS3} = 350 mV$$

$$\begin{aligned} \text{Constanta de proces: } \mu C_{ox} &= \frac{2 I_{Dref} \cdot L_{ref}}{W_{ref} \cdot V_{DSatref}^2} = \frac{2 \cdot 50 \mu A \cdot 1 \mu}{5 \mu (200 mV)^2} = \frac{100 \mu A}{288000 \cdot 10^{-6} V^2} = \\ &= \frac{100 \mu A}{0,288 V^2} = 345,22 \frac{\mu A}{V^2} \end{aligned}$$

Tranzistor	$W/L$	$I_D$	$V_{DSat}$	$V_{DS}$	$V_{Th}$	$V_{GS}$	$g_m$	$g_{DS}$
$M_1$	$3,16 \mu / 1 \mu$	$15 \mu A$	$203 mV$	$665 mV$	$446 mV$	$665 mV$	$114 \mu S$	$1,38 \mu S$
$M_2$	$3,0 \mu / 1 \mu$	$15 \mu A$	$200 mV$	$853 mV$	$622 mV$	$853 mV$	$117 \mu S$	$1,28 \mu S$
$M_3$	$3,16 \mu / 1 \mu$	$15 \mu A$	$203 mV$	$660 mV$	$446 mV$	$665 mV$	$114 \mu S$	$1,38 \mu S$
$M_4$	$3,72 \mu / 1 \mu$	$15 \mu A$	$200 mV$	$340 mV$	$620 mV$	$858 mV$	$119 \mu S$	$2,06 \mu S$

Ajustări:

$$\text{pentru } M_2 \rightarrow W = 3,0 \mu$$

$$AS = AD = 0,52 \mu m^2$$

$$PS = PD = 5,6 \mu m$$

$$\text{pentru } M_4 \rightarrow W = 3,72 \mu$$

$$AS = AD = 0,54 \mu m^2$$

$$PS = PD = 5,84 \mu m$$

$$R_{in} = \frac{1}{g_{m1}} + \frac{1}{g_{m2}} = \frac{1}{114} \cdot 10^6 + \frac{1}{117} \cdot 10^6 = 17,1 K\Omega \rightarrow \text{Calculat}$$

$$R_{in} = \frac{1}{S_{lope}} = \frac{1}{52} \cdot 10^6 = 0,0192 \cdot 10^6 = 19,2 K\Omega \rightarrow \text{Măsurat}$$



## • Error log inainte de ajustare

```

SPICE Error Log: C:\Users\ASUS\OneDrive\Desktop\cia\Proiect_noi\oglinda\ogl-cascodaLV-MOS.log
Circuit: * C:\Users\ASUS\OneDrive\Desktop\cia\Proiect_noi\oglinda\ogl-cascodaLV-MOS.asc


Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
    --- BSIM3 MOSFETS ---
Name:      m1      m3      m2      m4
Model:     n018     n018     n018     n018
Id:        1.50e-05  1.50e-05  1.50e-05  1.50e-05
Vgs:       6.65e-01  6.65e-01  8.53e-01  8.58e-01
Vds:       6.65e-01  6.60e-01  8.53e-01  3.40e-01
Vbs:       0.00e+00  0.00e+00  -6.65e-01 -6.60e-01
Vth:       4.46e-01  4.46e-01  6.22e-01  6.20e-01
Vdsat:     2.03e-01  2.03e-01  2.18e-01  2.23e-01
Gm:        1.14e-04  1.14e-04  1.07e-04  1.05e-04
Gds:       1.38e-06  1.38e-06  1.23e-06  2.22e-06
Gmb:       3.64e-05  3.64e-05  2.80e-05  2.74e-05
Cbd:       4.30e-15  4.31e-15  3.66e-15  4.00e-15
Cbs:       5.30e-15  5.30e-15  4.30e-15  4.31e-15
Cgsov:     1.18e-15  1.18e-15  1.18e-15  1.18e-15
Cgdov:     1.17e-15  1.17e-15  1.17e-15  1.18e-15
Cgbov:     0.00e+00  0.00e+00  0.00e+00  0.00e+00
dQgdVgb:   1.60e-14  1.60e-14  1.58e-14  1.59e-14
dQgdVdb:   -1.17e-15 -1.17e-15 -1.17e-15 -1.28e-15
dQgdVsb:   -1.39e-14 -1.39e-14 -1.39e-14 -1.40e-14
dQddVgb:   -1.20e-15 -1.20e-15 -1.18e-15 -1.43e-15
dQddVdb:   5.48e-15  5.49e-15  4.83e-15  5.41e-15
dQddVsb:   2.37e-17  2.41e-17  1.33e-17  8.26e-17
dQbdVgb:   -2.29e-15 -2.29e-15 -2.13e-15 -2.07e-15
dQbdVdb:   -4.30e-15 -4.31e-15 -3.66e-15 -4.06e-15
dQbdVsb:   -7.43e-15 -7.43e-15 -5.57e-15 -5.60e-15

Date: Sun May 08 15:09:03 2022
Total elapsed time: 0.059 seconds.

tnom = 27
temp = 27
method = trap
totiter = 6
traniter = 0
tranpoints = 0
accept = 0
rejected = 0
matrix size = 5
fillins = 0
solver = Normal
Matrix Compiler1: 248 bytes object code size
Matrix Compiler2: 389 bytes object code size

```

- Caracteristica de intrare

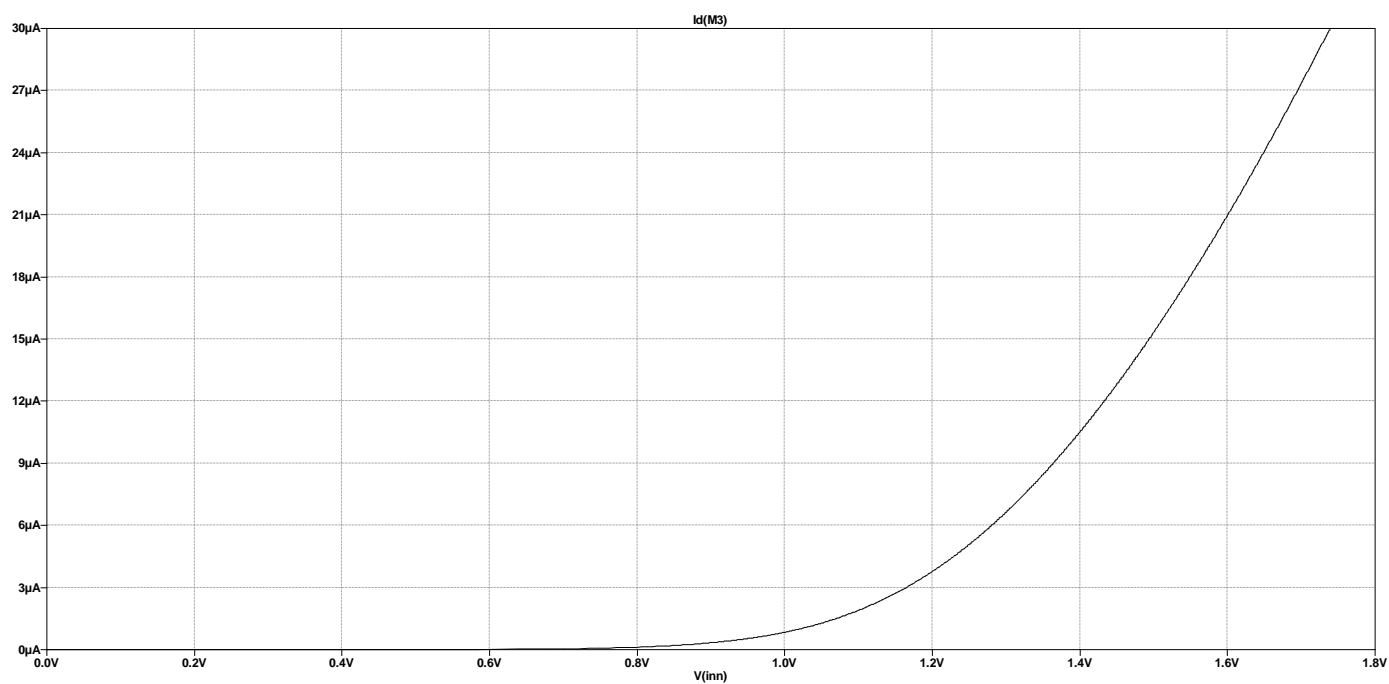

# PMOS

- Proiectarea circuitului după specificații ( $I_{in}$ ,  $I_{out}$ ,  $V_{dsat}$ )

Oglindă de curent

Topologie: Oglindă de curent cascadă PMOS

$$I_{in} = I_D = 15 \mu A$$

$$V_{DSat} = 200 mV$$

$$\frac{W}{L} = \left( \frac{W}{L} \right)_{neg} \cdot \frac{I_D}{I_{Dneg}} \cdot \left( \frac{V_{DSat neg}}{V_{DSat}} \right)^2 = \frac{15}{1} \cdot \frac{15}{50} \cdot \left( \frac{250}{200} \right)^2 = \frac{7,92}{1} \mu$$

$$A_S = A_D = 1,48 \mu m^2$$

$$P_S = P_D = 15,24 \mu m$$

$$V_{GS1} = V_{DSat1} + V_{Th} = 200 + 450 = 650 mV$$

Sim condiția de saturație a tranzistorului  $M_1$  rezultă că:

$$V_{DS1} > V_{DSat1} \Rightarrow V_{DS1} = 1,5 \cdot V_{DSat1} = 300 mV \Rightarrow V_{DS3} = V_{GS1} - V_{DS3} = 350 mV$$

$$\text{Constanta de proces: } \mu C_{ox} = \frac{2 I_{Dneg} \cdot L_{neg}}{W_{neg} \cdot V_{DSat neg}^2} = \frac{2 \cdot 50 \mu A \cdot 1 \mu}{15 \mu (250 mV)^2} = \frac{100 \mu A}{930235 \cdot 10^{-6} V^2} = \frac{100 \mu A}{0,93 V^2} \approx 101 \mu A/V^2$$

Tranzistor	$W/L$	$I_D$	$V_{DSat}$	$V_{DS}$	$V_{Th}$	$V_{GS}$	$g_m$	$g_{DS}$
$M_1$	$7,92 \mu / 1 \mu$	$15 \mu A$	$204 mV$	$731 mV$	$446 mV$	$731 mV$	$103 \mu S$	$1,84 \mu S$
$M_2$	$7,92 \mu / 1 \mu$	$15 \mu A$	$200 mV$	$881 mV$	$628 mV$	$881 mV$	$113 \mu S$	$1,72 \mu S$
$M_3$	$7,92 \mu / 1 \mu$	$15 \mu A$	$204 mV$	$731 mV$	$446 mV$	$731 mV$	$103 \mu S$	$1,84 \mu S$
$M_4$	$7,92 \mu / 1 \mu$	$15 \mu A$	$200 mV$	$269 mV$	$628 mV$	$881 mV$	$113 \mu S$	$4,58 \mu S$

Ajustări:


$$\begin{aligned} \text{- pentru } M_2 \rightarrow W &= 8,8 \mu \\ A_S &= A_D = 1,76 \mu m^2 \\ P_S &= P_D = 18 \mu m \end{aligned}$$

$$\begin{aligned} \text{- pentru } M_4 \rightarrow W &= 8,6 \mu \\ A_S &= A_D = 1,52 \mu m^2 \\ P_S &= P_D = 15,6 \mu m \end{aligned}$$

$$R_{out} = r_{DS3} + r_{DS4} + (g_{m1} + g_{m4}) r_{DS3} r_{DS4} = 543 k + 218 k + (113 \mu + 24,5 \mu) 543 k \cdot 218 k = 16,3 M\Omega \rightarrow \text{calculat}$$

$$R_{out} = \frac{1}{\text{slope}} = \frac{1}{63 \cdot 10^{-9}} = 15,8 M\Omega$$

## Schema de proiectare a circuitului

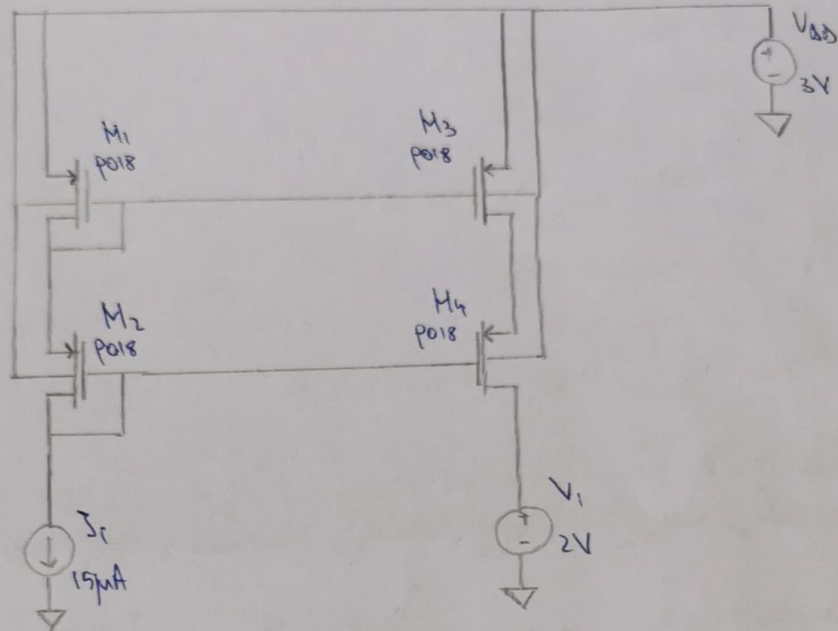

## • Error log înainte de ajustare

SPICE Error Log: C:\Users\ASUS\OneDrive\Desktop\cia\Proiect\_noi\og Linda\de tip p\ogl-cascodaP-MOS.log

Circuit: \* C:\Users\ASUS\OneDrive\Desktop\cia\Proiect\_noi\og Linda\de tip p\ogl-cascodaP-MOS.asc

Direct Newton iteration for .op point succeeded.

Semiconductor Device Operating Points:

--- BSIM3 MOSFETS ---			
Name:	m1	m2	m3
Model:	p018	p018	p018
Id:	-1.50e-05	-1.50e-05	-1.50e-05
Vgs:	-7.31e-01	-9.04e-01	-9.15e-01
Vds:	-7.31e-01	-9.04e-01	-2.80e-01
Vbs:	0.00e+00	7.31e-01	7.20e-01
Vth:	-4.46e-01	-6.28e-01	-6.26e-01
Vdsat:	-2.04e-01	-2.16e-01	-2.25e-01
Gm:	1.03e-04	1.02e-04	9.58e-05
Gds:	1.84e-06	1.68e-06	5.25e-06
Gmb:	2.79e-05	2.24e-05	2.10e-05
Cbd:	1.80e-14	1.46e-14	1.69e-14
Cbs:	2.40e-14	1.80e-14	1.81e-14
Cgsov:	4.04e-15	4.04e-15	4.04e-15
Cgdov:	4.00e-15	4.00e-15	4.04e-15
Cgbv:	0.00e+00	0.00e+00	0.00e+00
dqgdVgb:	5.56e-14	5.46e-14	5.53e-14
dqgdVdb:	-4.01e-15	-4.00e-15	-4.89e-15
dqgdVsb:	-4.90e-14	-4.84e-14	-4.83e-14
dqddVgb:	-4.08e-15	-4.05e-15	-5.92e-15
dqddVdb:	2.21e-14	1.87e-14	2.31e-14
dqddVsb:	5.55e-17	3.56e-17	-3.75e-17
dqbdVgb:	-9.55e-15	-8.61e-15	-8.07e-15
dqbdVdb:	-1.80e-14	-1.46e-14	-1.75e-14
dqbdVsb:	-2.82e-14	-1.99e-14	-2.00e-14

Date: Sun May 08 18:01:10 2022

Total elapsed time: 0.048 seconds.

tnom = 27

temp = 27

method = trap

totiter = 7

traniter = 0

tranpoints = 0

accept = 0

rejected = 0

matrix size = 7


fillins = 0

solver = Normal



Matrix Compiler1: 348 bytes object code size

Matrix Compiler2: 623 bytes object code size

- Caracteristica de iesire

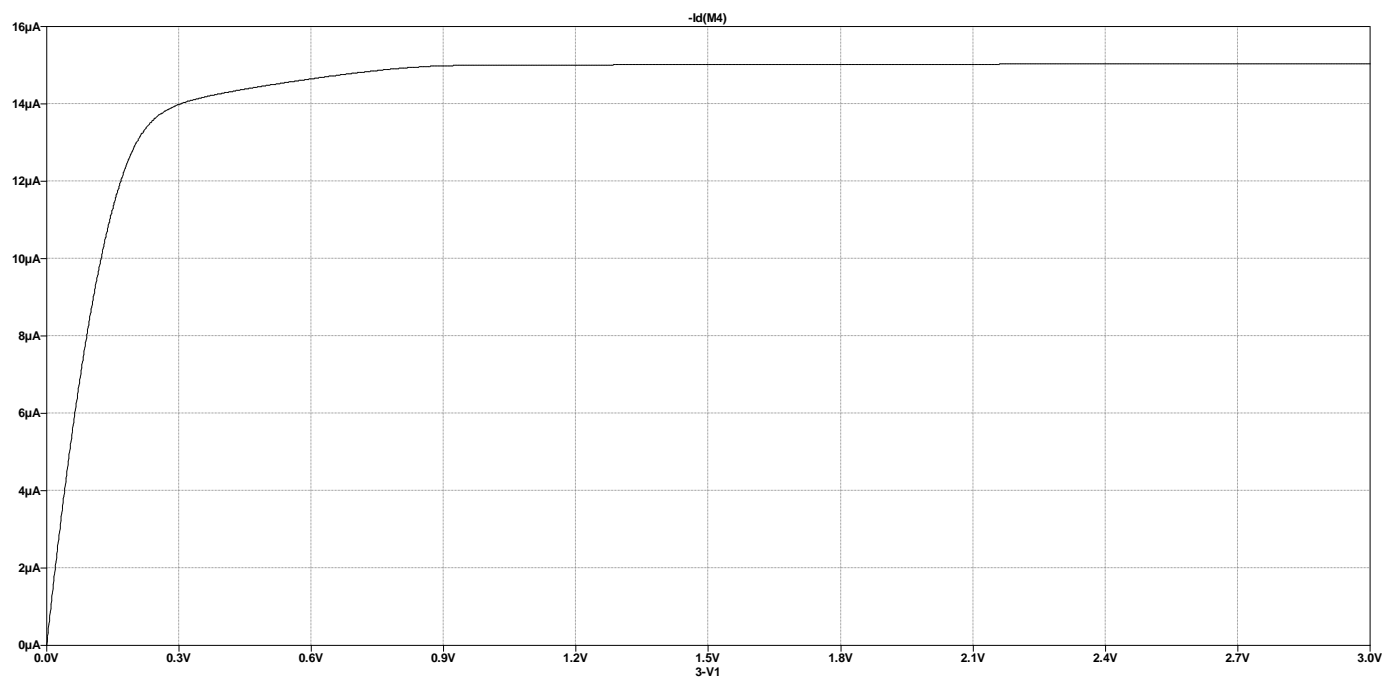

# Raport circuit final

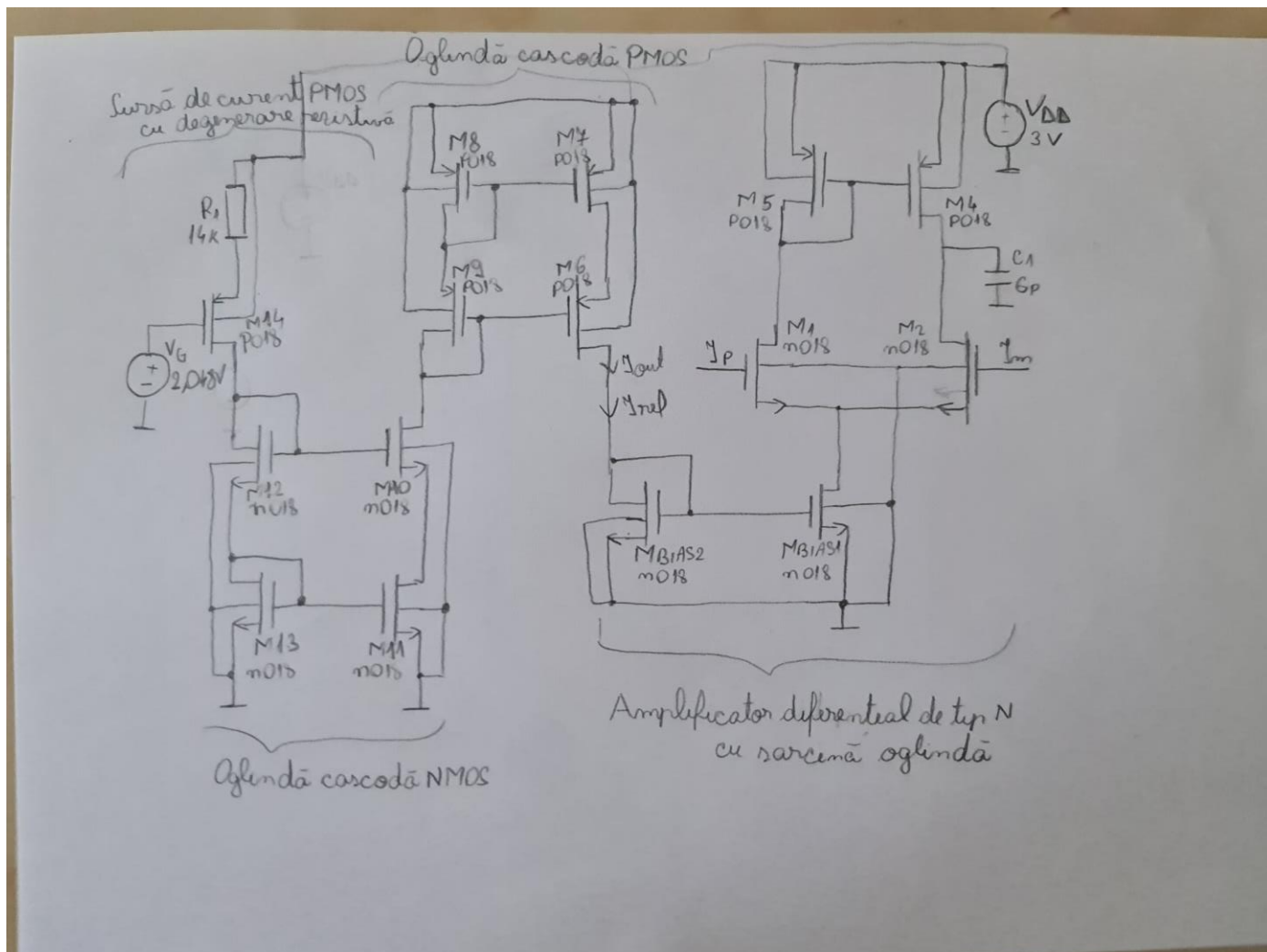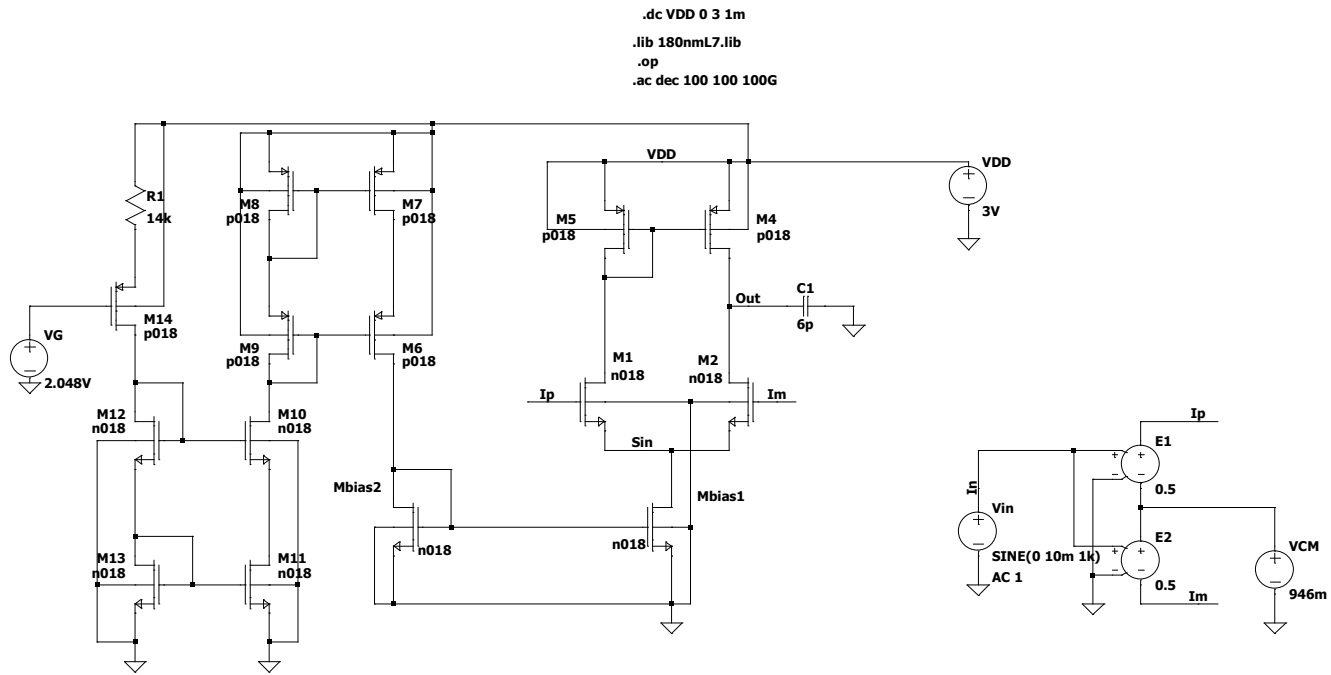



## • Error log inainte de ajustare

```
SPICE Error Log: C:\Users\ASUS\OneDrive\Desktop\cia\Proiect_noi\Toate\Proiect_final.log
Circuit: * C:\Users\ASUS\OneDrive\Desktop\cia\Proiect_noi\Toate\Proiect_final.asc

Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM3 MOSFETS ---
Name: m14 m9 m8 m7 m6
Model: p018 p018 p018 p018 p018
Id: -1.43e-05 -1.43e-05 -1.43e-05 -1.43e-05 -1.43e-05
Vgs: -7.52e-01 -8.73e-01 -7.24e-01 -7.24e-01 -8.56e-01
Vds: -1.32e+00 -8.73e-01 -7.24e-01 -7.40e-01 -1.60e+00
Vbs: 2.00e-01 7.24e-01 0.00e+00 0.00e+00 7.40e-01
Vth: -5.01e-01 -6.27e-01 -4.46e-01 -4.46e-01 -6.30e-01
Vdsat: -1.88e-01 -1.96e-01 -1.99e-01 -1.99e-01 -1.81e-01
Gm: 1.11e-04 1.11e-04 1.01e-04 1.01e-04 1.22e-04
Gds: 1.62e-06 1.65e-06 1.76e-06 1.76e-06 1.53e-06
Gmb: 2.81e-05 2.42e-05 2.73e-05 2.74e-05 2.64e-05
Cbd: 1.12e-14 1.74e-14 1.81e-14 1.80e-14 1.68e-14
Cbs: 1.63e-14 2.13e-14 2.40e-14 2.40e-14 2.31e-14
Cgsow: 4.48e-15 4.79e-15 4.04e-15 4.04e-15 5.23e-15
Cgdov: 4.16e-15 4.74e-15 4.00e-15 3.99e-15 4.78e-15
Cgbov: 0.00e+00 0.00e+00 0.00e+00 0.00e+00 0.00e+00
dqgdVgb: 6.10e-14 6.48e-14 5.56e-14 5.56e-14 7.02e-14
dqgdVdb: -4.16e-15 -4.75e-15 -4.01e-15 -4.01e-15 -4.78e-15
dqgdVsb: -5.40e-14 -5.73e-14 -4.90e-14 -4.90e-14 -6.25e-14
dqgdVgb: -4.18e-15 -4.80e-15 -4.08e-15 -4.07e-15 -4.80e-15
dqgdVdb: 1.54e-14 2.22e-14 2.21e-14 2.20e-14 2.16e-14
dqgdVsb: 1.89e-17 4.49e-17 5.66e-17 5.42e-17 1.44e-17
dqbdVgb: -1.02e-14 -1.02e-14 -9.55e-15 -9.56e-15 -1.12e-14
dqbdVdb: -1.12e-14 -1.74e-14 -1.81e-14 -1.80e-14 -1.68e-14
dqbdVsb: -2.01e-14 -2.37e-14 -2.82e-14 -2.82e-14 -2.56e-14

Name: m5 m4 m13 m12 m11
Model: p018 p018 n018 n018 n018
Id: -3.60e-04 -3.60e-04 1.43e-05 1.43e-05 1.43e-05
Vgs: -7.26e-01 -7.26e-01 6.58e-01 8.21e-01 6.58e-01
Vds: -7.26e-01 -7.26e-01 6.58e-01 8.21e-01 6.62e-01
Vbs: 0.00e+00 0.00e+00 0.00e+00 -6.58e-01 0.00e+00
Vth: -4.46e-01 -4.46e-01 4.46e-01 6.20e-01 4.46e-01
Vdsat: -2.01e-01 -2.01e-01 1.98e-01 1.95e-01 1.98e-01
Gm: 2.51e-03 2.51e-03 1.11e-04 1.16e-04 1.11e-04
Gds: 4.43e-05 4.43e-05 1.32e-06 1.23e-06 1.32e-06
Gmb: 6.82e-04 6.82e-04 3.54e-05 2.99e-05 3.55e-05
Cbd: 4.37e-13 4.37e-13 4.31e-15 4.39e-15 4.30e-15
Cbs: 5.81e-13 5.81e-13 5.30e-15 5.14e-15 5.30e-15
Cgsow: 1.00e-13 1.00e-13 1.18e-15 1.42e-15 1.18e-15
Cgdov: 9.90e-14 9.90e-14 1.17e-15 1.40e-15 1.17e-15
Cgbov: 0.00e+00 0.00e+00 0.00e+00 0.00e+00 0.00e+00
dqgdVgb: 1.38e-12 1.38e-12 1.60e-14 1.90e-14 1.60e-14
dqgdVdb: -9.94e-14 -9.94e-14 -1.17e-15 -1.41e-15 -1.17e-15
dqgdVsb: -1.21e-12 -1.21e-12 -1.39e-14 -1.67e-14 -1.39e-14
dqbdVgb: -1.01e-13 -1.01e-13 -1.20e-15 -1.42e-15 -1.20e-15
dqbdVdb: 5.37e-13 5.37e-13 5.49e-15 5.80e-15 5.48e-15
dqbdVsb: -6.85e-13 -6.85e-13 -7.43e-15 -6.67e-15 -7.43e-15

Name: m10 mbias2 m2 mbias1 m1
Model: n018 n018 n018 n018 n018
Id: 1.43e-05 1.43e-05 3.60e-04 7.20e-04 3.60e-04
Vgs: 8.17e-01 6.59e-01 7.15e-01 6.59e-01 7.15e-01
Vds: 7.41e-01 6.59e-01 2.04e+00 2.31e-01 2.04e+00
Vbs: -6.62e-01 0.00e+00 -2.31e-01 0.00e+00 -2.31e-01
Vth: 6.21e-01 4.46e-01 5.12e-01 4.46e-01 5.12e-01
Vdsat: 1.92e-01 1.98e-01 1.94e-01 1.99e-01 1.94e-01
Gm: 1.18e-04 1.11e-04 2.84e-03 5.46e-03 2.84e-03
Gds: 1.25e-06 1.33e-06 2.88e-05 3.66e-04 2.88e-05
Gmb: 3.04e-05 3.55e-05 8.36e-04 1.75e-03 8.36e-04
Cbd: 4.62e-15 4.31e-15 7.79e-14 1.70e-07 7.79e-14
Cbs: 5.35e-15 5.30e-15 1.15e-13 2.67e-13 1.15e-13
Cgsow: 1.48e-15 1.18e-15 2.95e-14 6.30e-14 2.95e-14
Cgdov: 1.47e-15 1.17e-15 2.61e-14 6.30e-14 2.61e-14
Cgbov: 0.00e+00 0.00e+00 0.00e+00 0.00e+00 0.00e+00
dqgdVgb: 1.99e-14 1.60e-14 3.95e-13 8.70e-13 3.95e-13
dqgdVdb: -1.48e-15 -1.17e-15 -2.61e-14 -7.94e-14 -2.61e-14
dqgdVsb: -1.78e-14 -1.39e-14 -3.48e-13 -7.45e-13 -3.48e-13
dqbdVgb: -1.50e-15 -1.20e-15 -2.61e-14 -1.00e-13 -2.61e-14
dqbdVdb: 6.11e-15 5.49e-15 1.04e-13 1.70e-07 1.04e-13
dqbdVsb: 2.18e-17 2.40e-17 5.51e-17 7.80e-15 5.51e-17
dqbdVgb: -2.68e-15 -2.29e-15 -5.55e-14 -1.13e-13 -5.55e-14
dqbdVdb: -4.63e-15 -4.31e-15 -7.79e-14 -1.70e-07 -7.79e-14
dqbdVsb: -6.95e-15 -7.43e-15 -1.59e-13 -3.83e-13 -1.59e-13

Date: Tue May 10 19:10:54 2022
Total elapsed time: 0.044 seconds.

tnom = 27
temp = 27
method = trap
totiter = 8
traniter = 0
tranpoints = 0
accept = 0
rejected = 0
matrix size = 23
fillins = 0
solver = Normal
Matrix Compiler1: 1.36 KB object code size
Matrix Compiler2: 2.06 KB object code size
```

# • Tabel cu parametrii

Transistor	W/L	I <sub>D</sub>	V <sub>DSat</sub>	V <sub>DS</sub>	V <sub>Th</sub>	V <sub>GS</sub>	g <sub>m</sub>	g <sub>DS</sub>
Sursa de curent								
M14	9,6μ/1μ	15μA	180mV	1,30V	504mV	742mV	124μS	1,72μS
Oglindă de curent								
M12	2,6μ/1μ	15μA	200mV	823mV	622mV	823mV	118μS	1,29μS
M13	2,16μ/1μ	15μA	203mV	665mV	446mV	665mV	114μS	1,33μS
M11	2,16μ/1μ	15μA	203mV	668mV	446mV	665mV	114μS	1,37μS
M10	2,72μ/1μ	15μA	137mV	720mV	622mV	825mV	121μS	1,31μS
M9	8,8μ/1μ	15μA	200mV	881mV	628mV	881mV	163μS	1,72μS
M8	7,47μ/1μ	15μA	204mV	731mV	446mV	731mV	103μS	1,84μS
M7	7,47μ/1μ	15μA	204mV	748mV	446mV	731mV	103μS	1,83μS
M6	2,0μ/1μ	15μA	186mV	1,53V	632mV	864mV	124μS	1,61μS
Amplificator diferențial								
M5	13,86μ/1μ	376μA	205mV	732mV	446mV	732mV	2,56mS	46μS
M4	13,86μ/1μ	376μA	205mV	732mV	446mV	732mV	2,56mS	46μS
M1	54,14μ/1μ	376μA	138mV	2,04V	511mV	719mV	2,90mS	23,3μS
M2	54,14μ/1μ	376μA	138mV	2,04V	511mV	719mV	2,90mS	23,3μS
M10a2	2,16μ/1μ	15μA	203mV	665mV	446mV	665mV	114μS	1,33μS
M10a1	11,53μ/1μ	752μA	203mV	227mV	446mV	665mV	5,52mS	449μS

$$R_{out} = r_{DS} + R_t (g_{m1} + g_{m2}) r_{DS} = 581k + 11k + (124\mu + 31\mu) 581k \cdot 11k = 1,85k\Omega \rightarrow \text{Sursă de curent}$$

$$R_{in} = \frac{1}{g_{m13}} + \frac{1}{g_{m12}} = \frac{1}{114 \cdot 10^6} + \frac{1}{118 \cdot 10^6} = 8,72k\Omega + 8,47k\Omega = 17,24k\Omega \rightarrow \text{Oglindă LMOS}$$

$$R_{out} = r_{DS1} + r_{DS6} + (g_{m6} + g_{m6}) r_{DS1} r_{DS6} = 546k + 621k + (124\mu + 26,9\mu) 546k \cdot 621k = 5326k\Omega \rightarrow \text{Oglindă PMOS}$$

$$A_0 = g_{m1} (r_{DS2} || r_{DS4}) = 38,13 \rightarrow 31,6dB$$

$$GBW = 76,3kHz$$

$$BW = 2,01kHz$$

$$f_{p1} = 2,01kHz$$


$$f_{p2} = 67,5kHz$$

→ Amplificator


Parametru	Calculat	Măsurat
Sursă de curent		
R <sub>outs</sub>	1,85kΩ	1,15kΩ
Oglindă de curent		
R <sub>in0</sub>	17,24kΩ	13,6kΩ
R <sub>out0</sub>	53,26kΩ	42,9kΩ
Amplificator diferențial		
A <sub>0</sub>	31,6dB	31,7dB
f <sub>pol</sub>	2,01kHz	1,73kHz
GBW	76,3kHz	61,28kHz



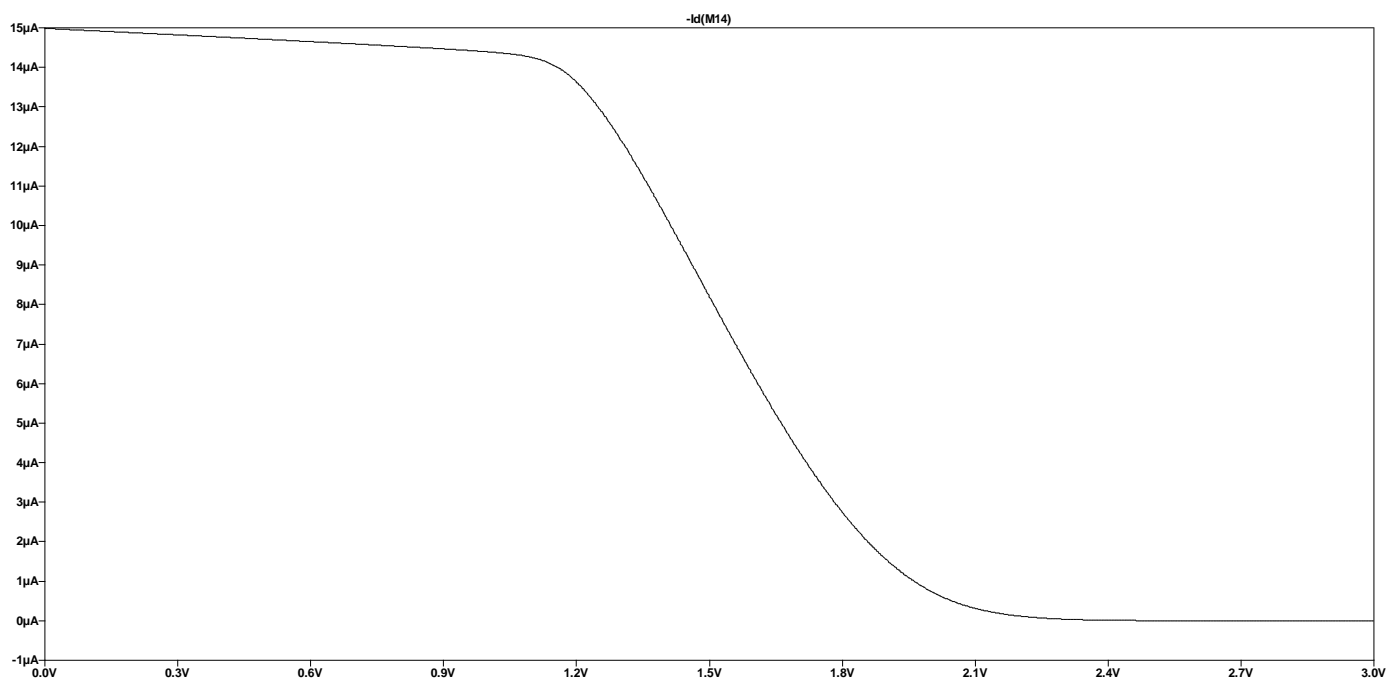
- Caracteristica de iesire a sursei de current



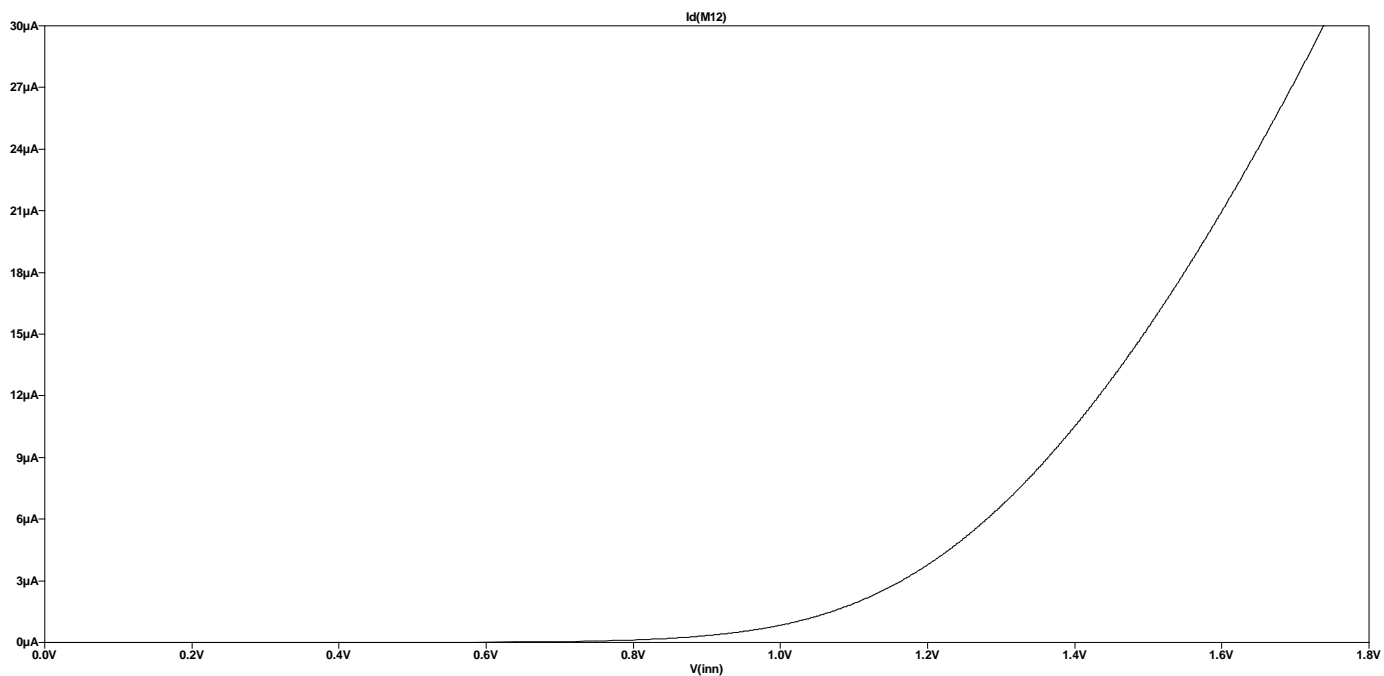
- Caracteristica de intrare a oglinzii de current



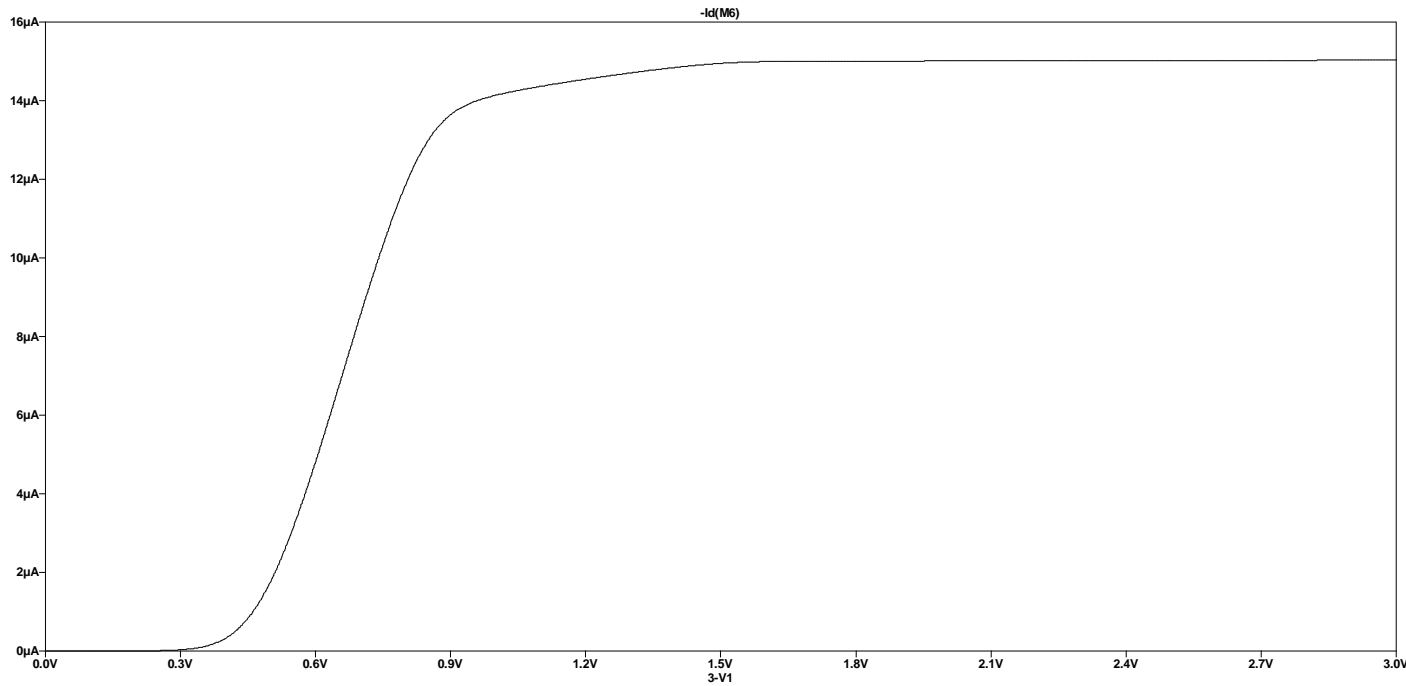- Caracteristica de iesire a oglinzii de current



- Caracteristica de modul si faza

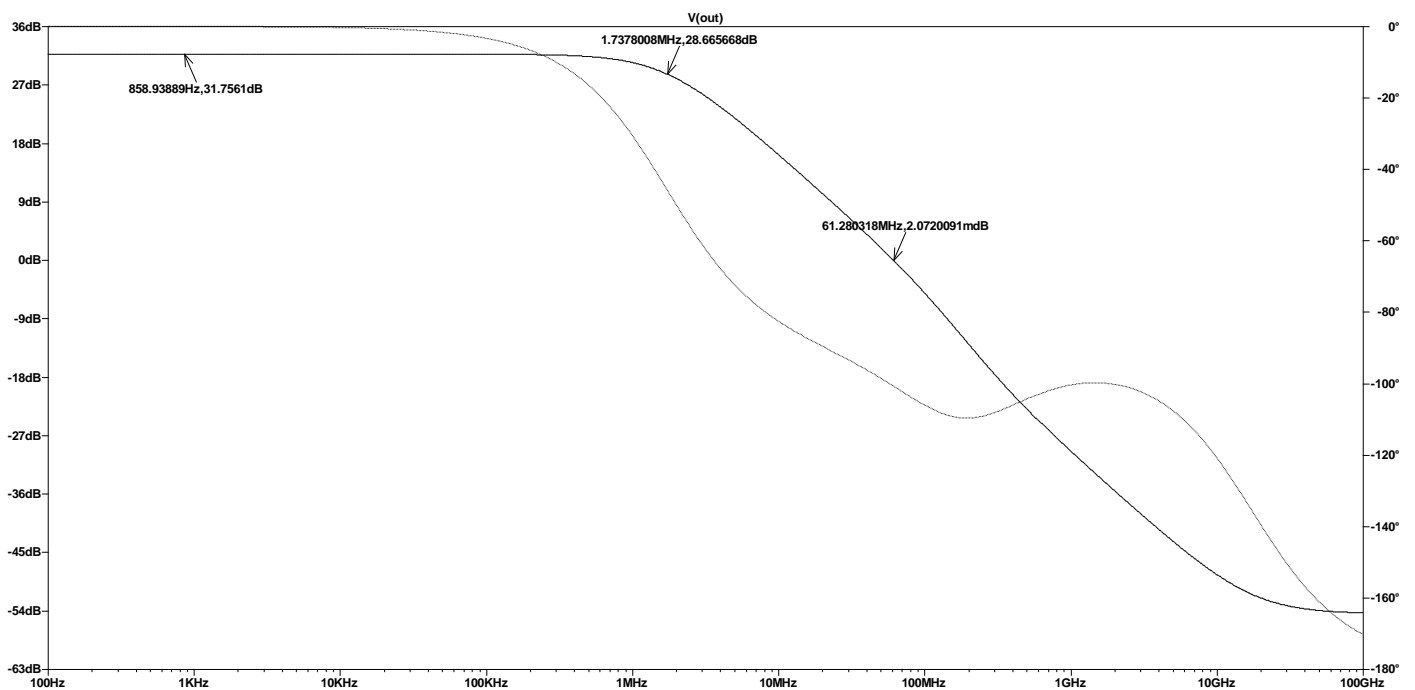

- Raspuns in timp al circuitului final

